

# Chapter 3 :: Sequential Logic Design (3)

## *Digital Design and Computer Architecture, 2<sup>nd</sup> Edition*


David Money Harris and Sarah L. Harris

# Chapter 3 :: Topics

- Introduction
- Latches and Flip-Flops
- Synchronous Logic Design
- **Finite State Machines**
- Shifter
- Timing of Sequential Logic
- Parallelism

 
## 3.4 1 Finite State Machine Example

- Traffic light controller
  - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - Lights:  $L_A$ ,  $L_B$




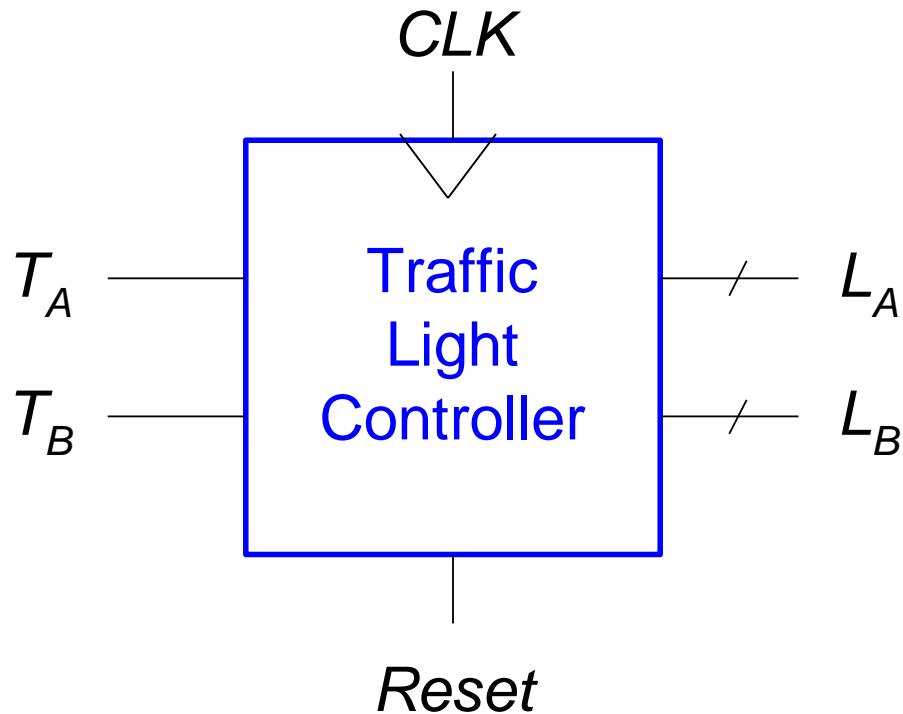
# FSM Black Box

- Inputs:  $CLK$ ,  $Reset$ ,  $T_A$ ,  $T_B$
- Outputs:  $L_A$ ,  $L_B$



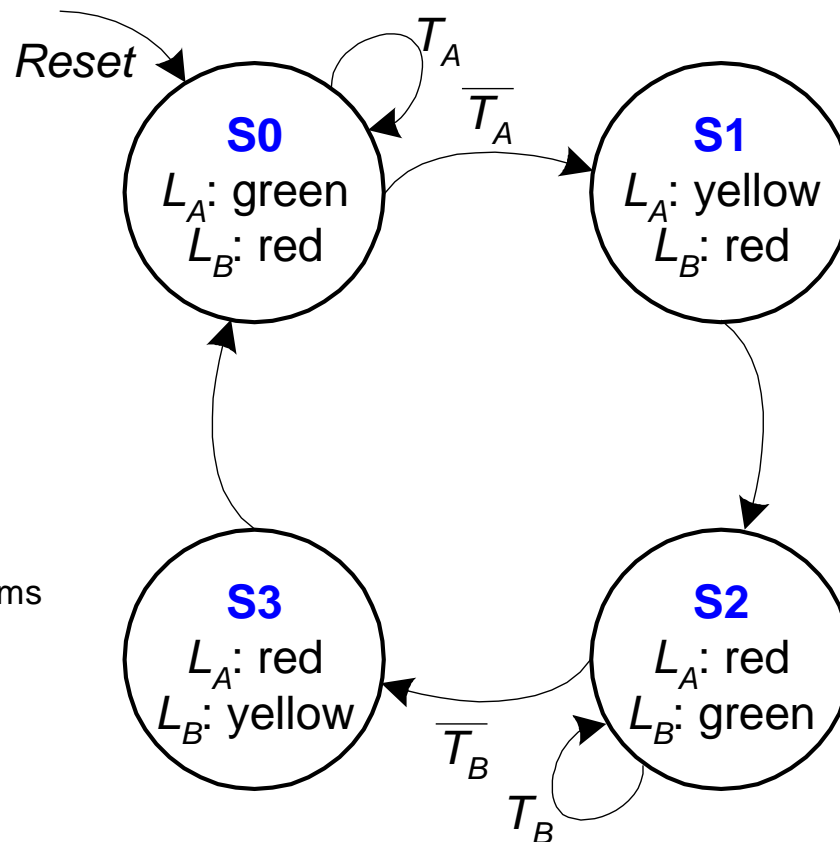 
# FSM State Transition Diagram

- Moore FSM: outputs labeled in each state
- States: Circles
- Transitions: Arcs



# FSM State Transition Table

 

Current State	Inputs		Next State
$S$	$T_A$	$T_B$	$S_{next}$
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

# FSM Encoded State Transition Table

Current State	Inputs		Next State
<i>State</i>	$T_A$	$T_B$	$S_{next}$
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding (2진 부호화)
S0	00
S1	01
S2	10
S3	11

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S_{1next}$	$S_{0next}$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

$$S_{1next} = S_1 \oplus S_0$$

$$S_{0next} = S_1' S_0' T_A' + S_1 S_0' T_B'$$

# FSM Output Table

Current State			Outputs			
State	$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
S0	0	0	0	0	1	0
S1	0	1	0	1	1	0
S2	1	0	1	0	0	0
S3	1	1	1	0	0	1


Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$

$$L_{A0} = S_1' S_0$$


$$L_{B1} = S_1'$$

$$L_{B0} = S_1 S_0$$

 




# FSM Schematic: State Register

 


# FSM Schematic: Next State Logic

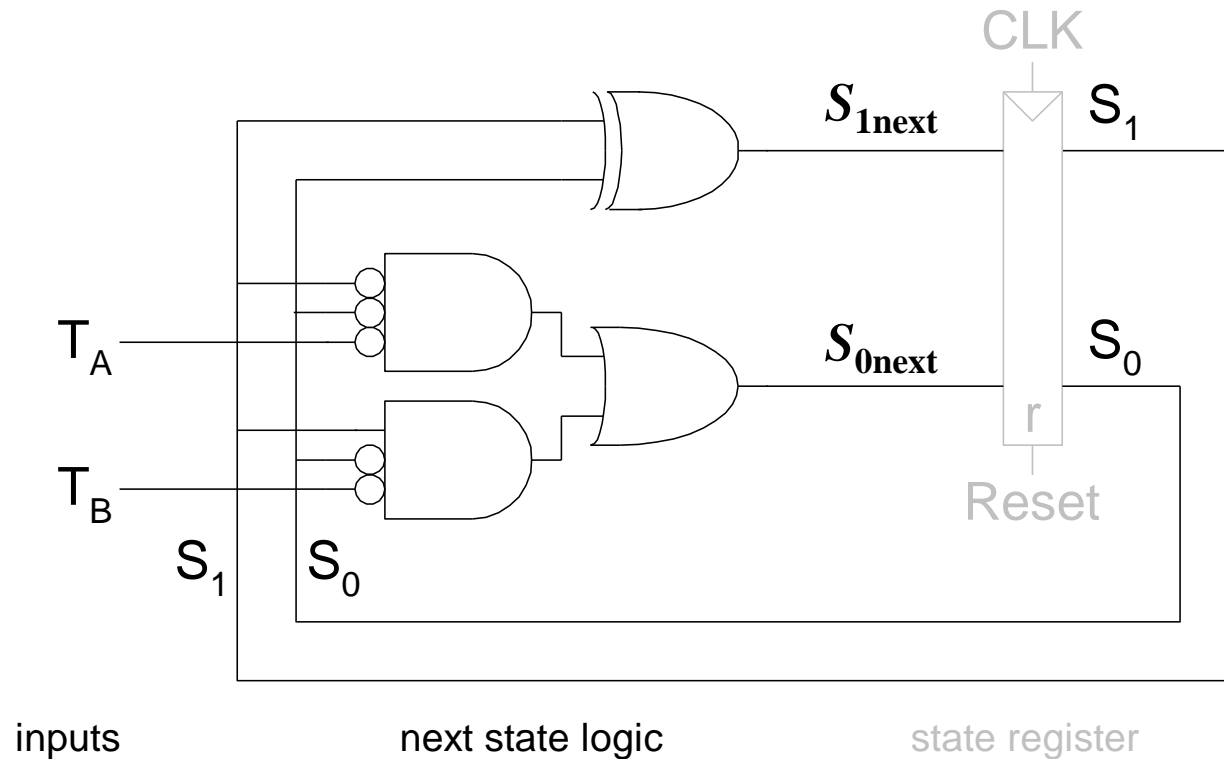

$$S_{1next} = S_1 \oplus S_0$$

$$S_{0next} = S_1' S_0' T_A' + S_1 S_0' T_B'$$

# FSM Schematic: Output Logic

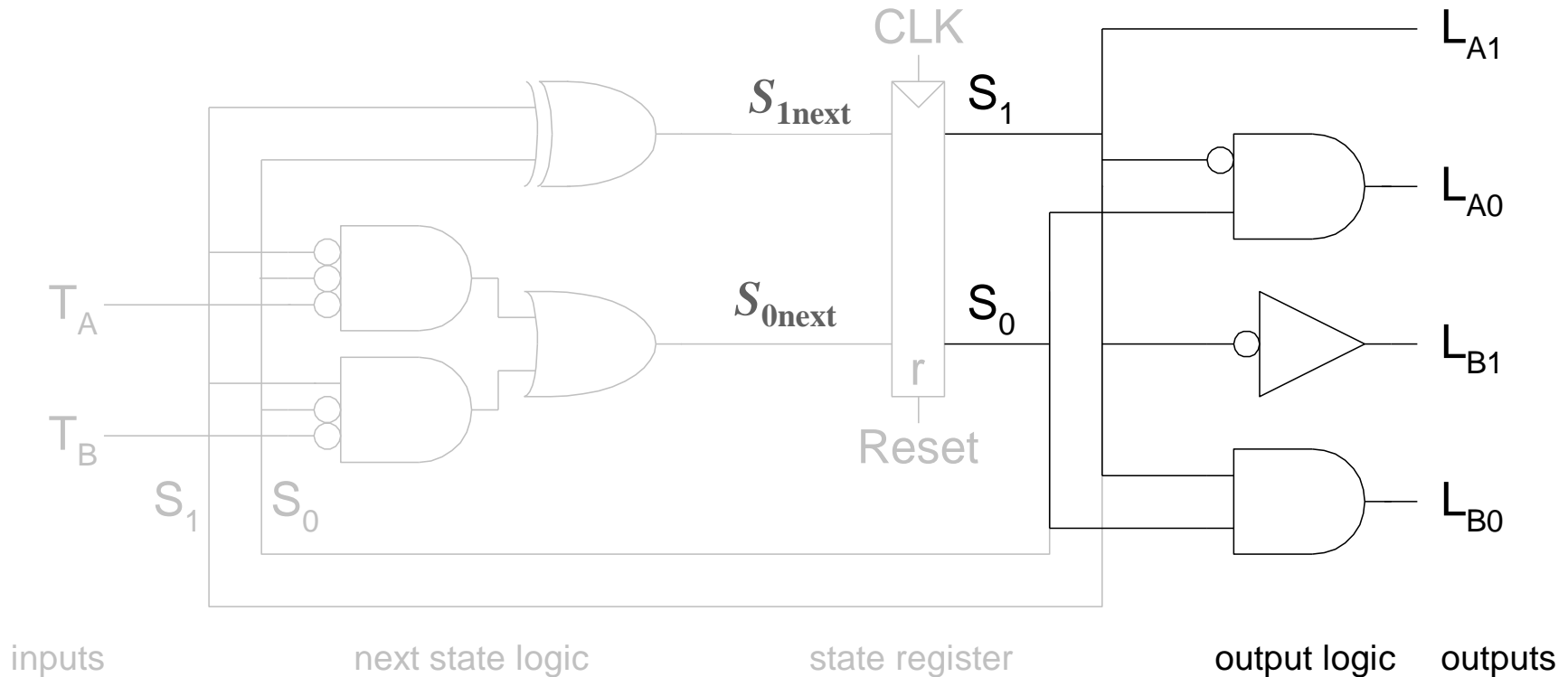


$$L_{A1} = S_1$$

$$L_{A0} = S_1' S_0$$

$$L_{B1} = S_1'$$

$$L_{B0} = S_1 S_0$$

# FSM Timing Diagram

 


## 3.4.2 FSM State Encoding(상태부호화)

- Binary encoding
  - i.e., for four states, 00, 01, 10, 11
- One-hot encoding
  - One state bit per state(각각의 상태를 위해 하나의 비트가 사용됨)
  - Only one state bit is HIGH at once(오직 하나의 비트만 참)
  - I.e., for four states, 0001, 0010, 0100, 1000
  - Requires more flip-flops(더 많은 수의 FF를 요구)
  - Often next state and output logic is simpler(다음 상태와 출력 논리는 더 간단)
 
## 예제 3.6 (p135)

- N진 카운터는 하나의 출력을 가지고 입력은 가지지 않는다. 출력 Y는 매 클록마다 하나의 클록 사이클 동안 HIGH 값이다. 이진 상태부호화와 one-hot 상태 부호화를 사용하여 회로를 설계하라.



© 2007 Elsevier, Inc. All rights reserved

표 3.6 3진 카운터의 상태 변이표	
현재 상태	다음 상태
S0	S1
S1	S2
S2	S0

표 3.7 3진 카운터의 출력표	
현재 상태	출력
S0	1
S1	0
S2	0

## 예제 3.6

표 3.8 divide-by-3 카운터를 위한 이진 부호화와 one-hot 부호화


State	One-Hot Encoding			Binary Encoding	
	$S_2$	$S_1$	$S_0$	$S_1$	$S_0$
S0	0	0	1	0	0
S1	0	1	0	0	1
S2	1	0	0	1	0

표 3.9 이진 부호화를 가진 상태 변이표

현재 상태		다음 상태	
$S_1$	$S_0$	$S'_1$	$S'_0$
0	0	0	1
0	1	1	0
1	0	0	0

표 3.10 one-hot 부호화를 가진 상태 변이표


현재 상태			다음 상태		
$S_2$	$S_1$	$S_0$	$S'_2$	$S'_1$	$S'_0$
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	0	0	1

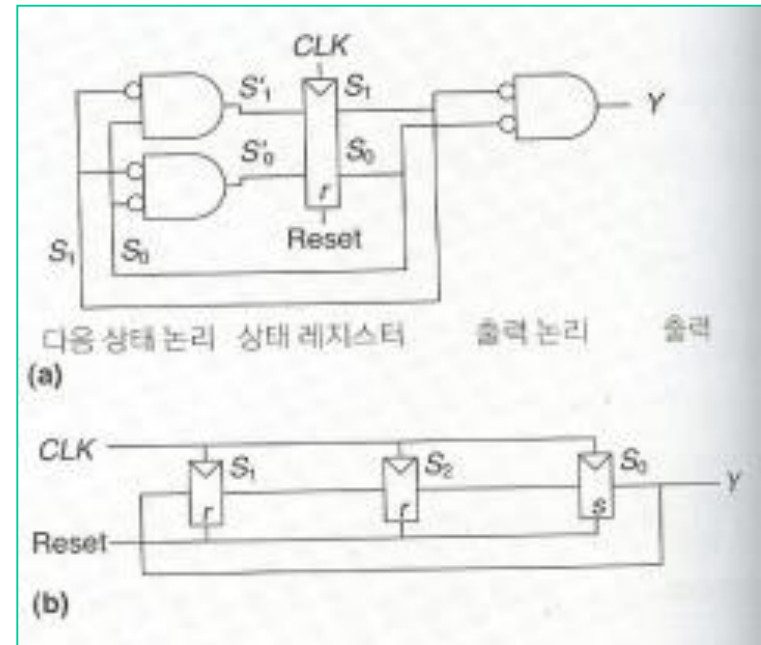

- $S'_2 = S_1$
- $S'_1 = S_0$
- $S'_0 = S_2$
- $Y'_1 = S_0$
 
### 3.4.3 Moore vs. Mealy FSM (**last four 1101**)


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The **snail smiles** whenever the **last four digits** it has crawled over are **1101**. Design Moore and Mealy FSMs of the snail's brain.





# State Transition Diagrams (**last four 1101**)


## Moore FSM

 

- 무어머신  
: 출력이 시스템 상태에만 의존  
: 출력을 원 안에

Mealy FSM: arcs indicate input/output

## Mealy FSM

 


- 밀리머신  
: 출력이 현재상태 및 입력에 의존  
: 출력을 화살표에

# Moore FSM State Transition Table

## (last four 1101)

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$		$Sn_2$	$Sn_1$	$Sn_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

 

# Moore FSM State Transition Table

## (last four 1101)

Current State			Inputs	Next State		
$S_2$	$S_1$	$S_0$		$Sn_2$	$Sn_1$	$Sn_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0

$S_0A$	00	01	11	10
$S_2S_1$				
00				
01			1	
11	X	X	X	X
10			X	X

- $Sn_2 = S_1S_0A$
- $Sn_1 = \overline{S_1}S_0A + S_1\overline{S_0} + S_2A$
- $Sn_0 = \overline{S_2}\overline{S_1}\overline{S_0}A + S_1\overline{S_0}\overline{A}$


# Moore FSM Output Table (**last four 1101**)

Current State			Output
$S_2$	$S_1$	$S_0$	$Y$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1


$$Y = S_2$$

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

Moore FSM

 

# Moore FSM Schematic (last four 1101)

 

- $S_{n2} = S_1 S_0 A$
- $S_{n1} = \overline{S_1} S_0 A + S_1 \overline{S_0} + S_2 A$
- $S_{n0} = \overline{S_2} \overline{S_1} \overline{S_0} A + S_1 \overline{S_0} \overline{A}$
- $Y = S_2$


# Mealy FSM State Transition and Output Table

## (last four 1101)

Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$S_{n1}$	$S_{n0}$	$Y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

State	Encoding
S0	00
S1	01
S2	10
S3	11

Mealy FSM

 


# Mealy FSM State Transition and Output Table (last four 1101)

Current State		Input	Next State		Output
$S_1$	$S_0$	$A$	$Sn_1$	$Sn_0$	$Y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

A	0	1
$S_1S_0$		
00		
01		1
11		
10	1	1

- $Sn_1 = S_1\bar{S}_0 + \bar{S}_1S_0A$
- $Sn_0 = \bar{S}_1\bar{S}_0A + S_1\bar{S}_0\bar{A} + S_1S_0A$
- $Y = S_1S_0A$

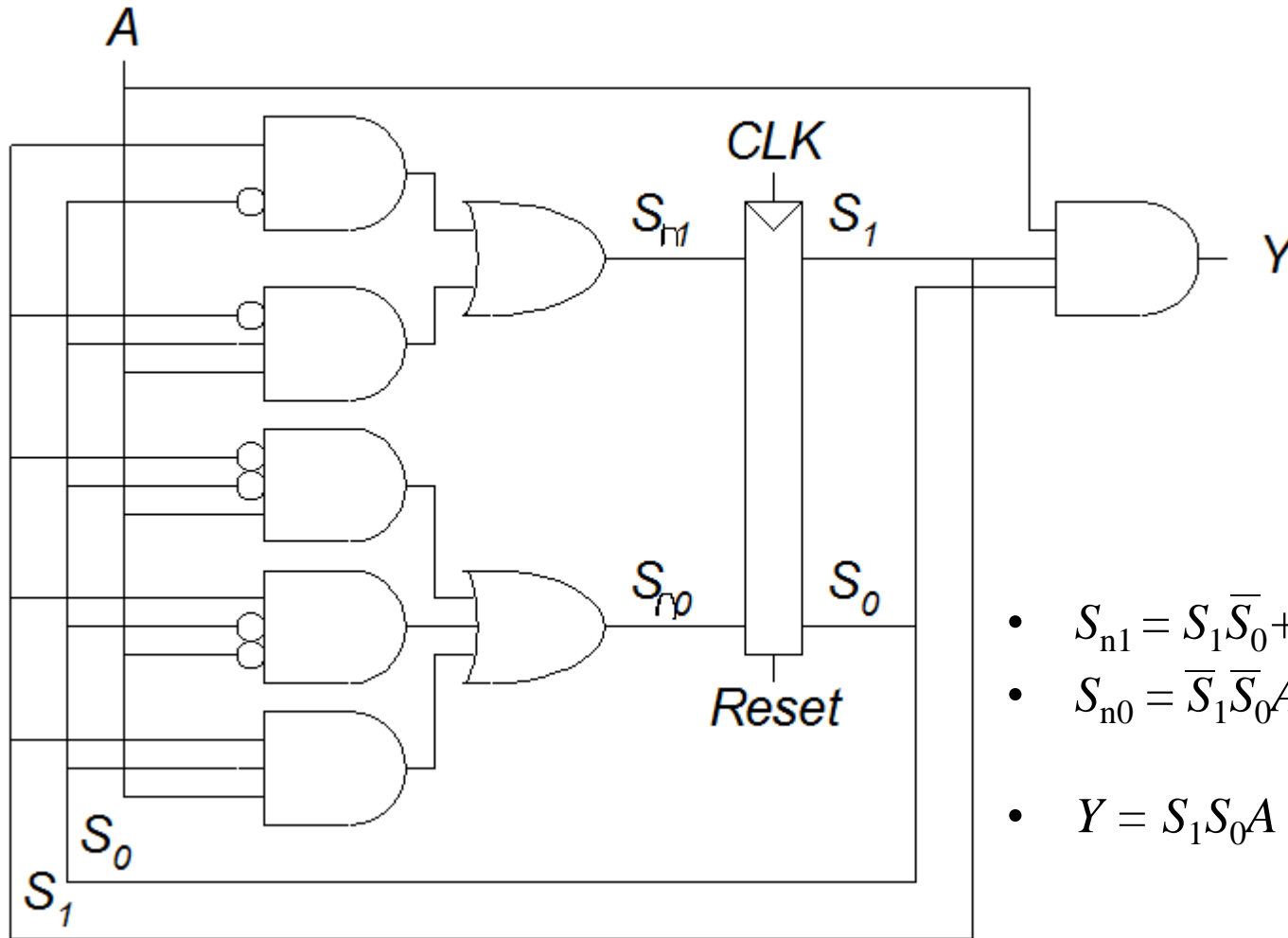
# Mealy FSM Schematic (**last four 1101**)



- $S_{n1} = S_1 \bar{S}_0 + \bar{S}_1 S_0 A$
- $S_{n0} = \bar{S}_1 \bar{S}_0 A + S_1 \bar{S}_0 \bar{A} + S_1 S_0 A$
- $Y = S_1 S_0 A$



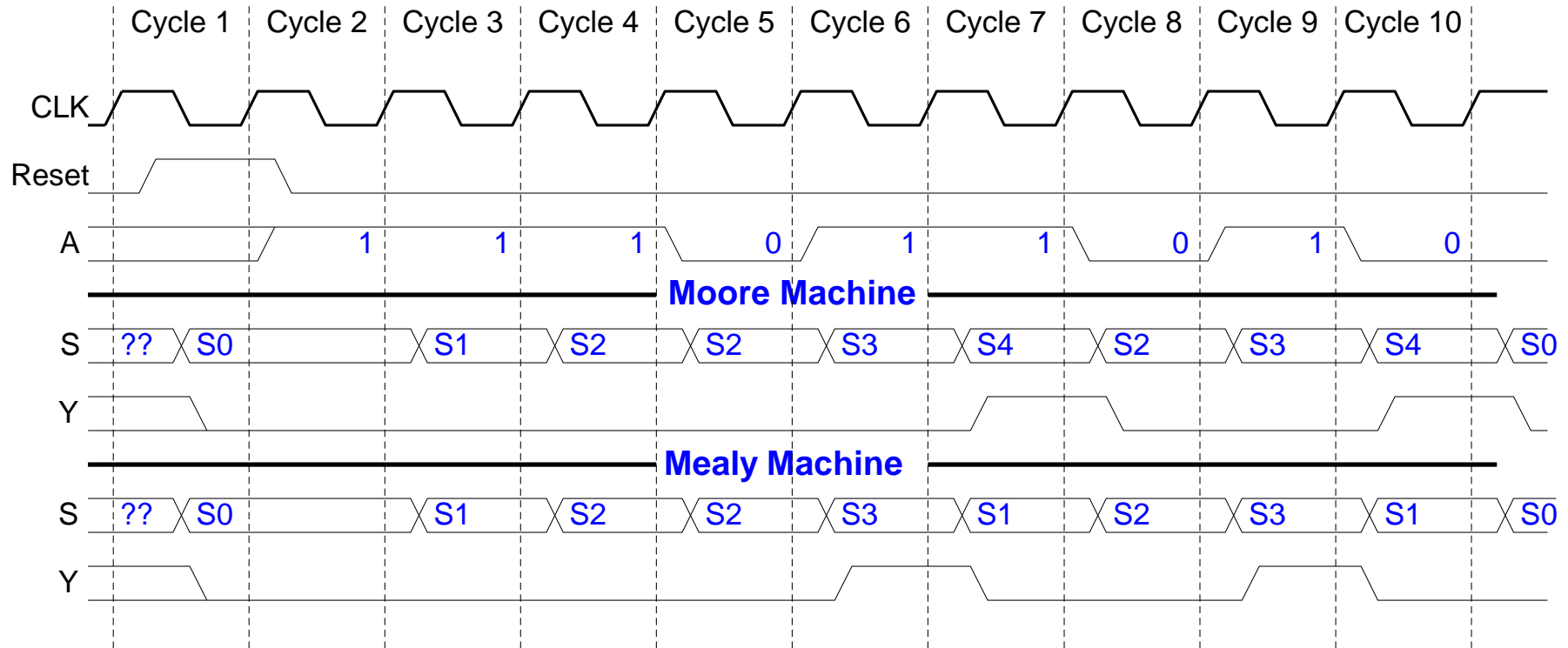
# Moore and Mealy Timing Diagram (last four 1101)



 
### 3.4.3 Moore vs. Mealy FSM (last two 01)

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The **snail smiles** whenever the last two digits it has crawled over are **01**. Design Moore and Mealy FSMs of the snail's brain.




# State Transition Diagrams (**last two 01**)

## Moore FSM

 

Mealy FSM: arcs indicate input/output

## Mealy FSM

 

# Moore FSM State Transition Table

## (last two 01)


Current State		Inputs	Next State	
$S_1$	$S_0$		$S'_1$	$S'_0$
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0

$$S'_1 = S_0 A$$

$$S'_0 = \overline{A}$$

State	Encoding
S0	00
S1	01
S2	10

### Moore FSM

 


# Moore FSM Output Table (**last two 01**)


$$Y = S_1$$

Current State		Output
$S_1$	$S_0$	$Y$
0	0	0
0	1	0
1	0	1

**Moore FSM**

 

# Moore FSM Schematic (last two 01)

 

$$S'_1 = S_0 A$$
$$S'_0 = \overline{S_0}$$

$$Y = S_1$$


# Mealy FSM State Transition and Output Table

(last two 01)


Current State	Input	Next State	Output
$S_0$	$A$	$S'_0$	$Y$
0	0	1	0
0	1	0	0
1	0	1	0
1	1	0	1

State	Encoding
S0	00
S1	01

## Mealy FSM

 


# Mealy FSM Schematic (**last two 01**)

 

- $S'_0 = \bar{A}$
- $Y = S_0 A$


 
# Moore and Mealy Timing Diagram (last two 01)




### 3.4.4 Factoring State Machines(상태머신 인수분해)


- Break complex FSMs into smaller interacting FSM  
(복잡한 FSM을 여러 개의 간단한 FSM으로 분류)
- Example
  - : Modify the traffic light controller to have a Parade Mode.
    - The FSM receives two more inputs:  $P$ ,  $R$
    - When  $P = 1$ , it enters Parade Mode and the Bravado Blvd. light stays green.
    - When  $R = 1$ , it leaves Parade Mode

# Parade FSM


## Unfactored FSM

 


## Factored FSM

 

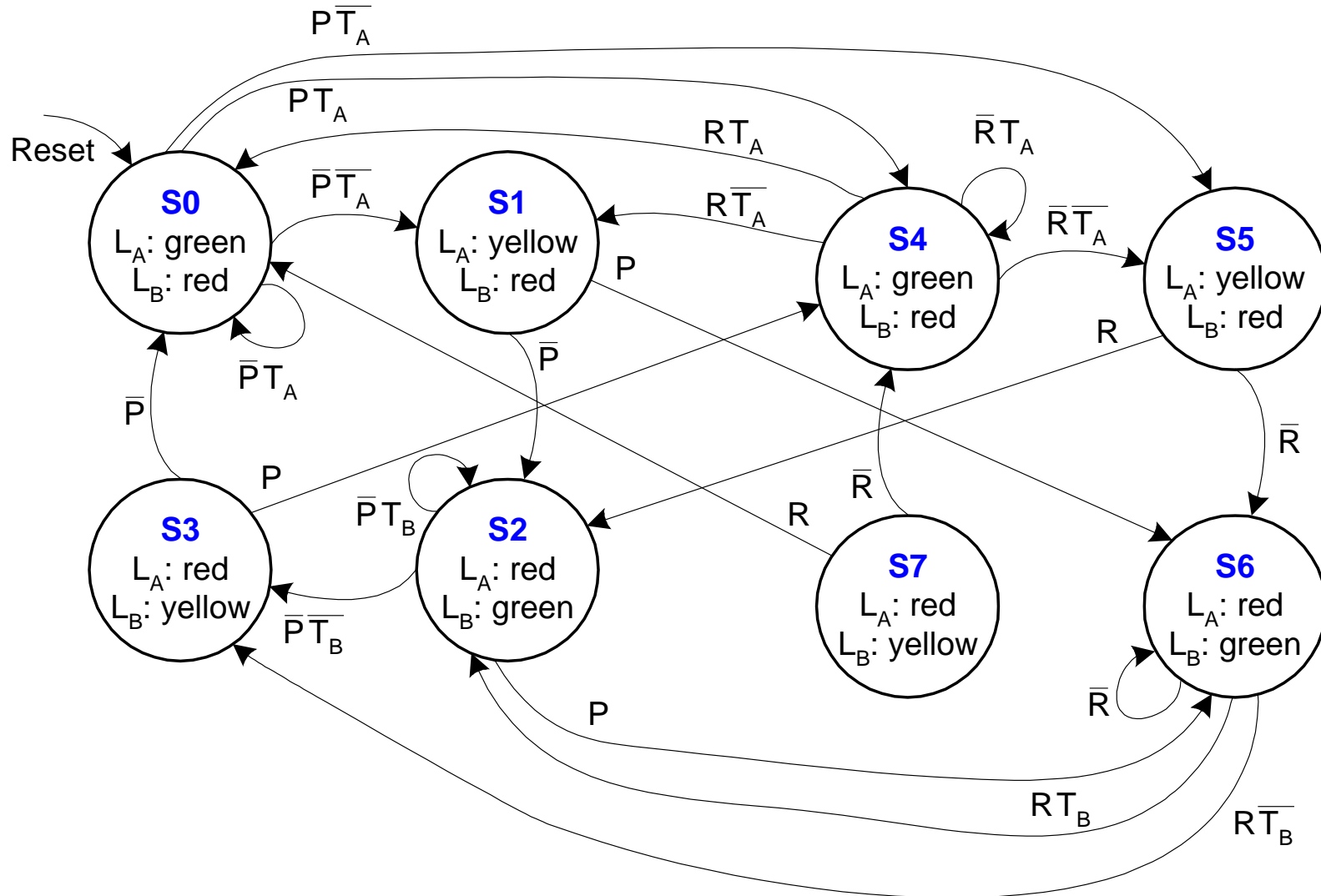
# Unfactored FSM State Transition Diagram



# Factored FSM State Transition Diagram

 


Lights FSM

 

Mode FSM

### 3.4.5 회로로부터 **FSM** 도출

- 실습시간에 분석

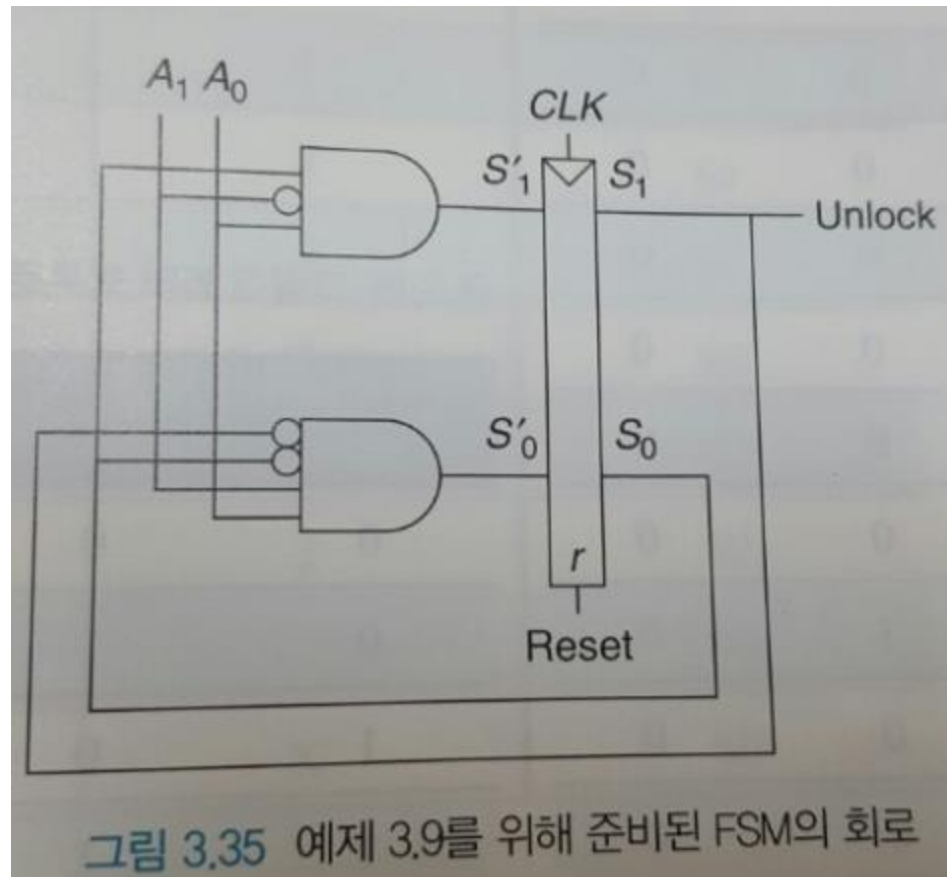

# Q & A

