

# Chapter 3 :: Sequential Logic Design (5)

## *Digital Design and Computer Architecture, 2<sup>nd</sup> Edition*

David Money Harris and Sarah L. Harris

참고도서 : 개정판 논리회로 설계(김종현저) , 홍릉과학출판사.

- 제7장 순차회로의 분석과 설계

# Chapter 3 :: Topics

- Introduction
- Latches and Flip-Flops
- Synchronous Logic Design
- Finite State Machines
- Shifter
  
- Timing of Sequential Logic
- Parallelism

# Timing (순차논리의 타이밍)


- Flip-flop samples  $D$  at clock edge
- $D$  must be stable when it is sampled
- Similar to a photograph,  $D$  must be stable around the clock edge
- If  $D$  is changing when it is sampled, metastability can occur

# Input Timing Constraints

- 전파 지연 시간(propagation delay time)
  - 플립-플롭에서 입력 신호가 인가된 순간부터 출력 신호가 발생할 때까지의 시간 간격 (내부 회로 동작 시간에 해당)
- Setup time
  - 플립-플롭의 출력 값이 안정된 상태로 결정되도록 하기 위하여, 입력 신호가 미리 세트 되어 있어야 하는 최소 시간
  - $t_{\text{setup}}$  = time *before* the clock edge that data must be stable (i.e. not changing)
- Hold time
  - 플립-플롭의 출력값이 안정된 상태로 결정되도록 하기 위하여, 입력 값이 그 상태를 유지하고 있어야 하는 최소 시간
  - $t_{\text{hold}}$  = time *after* the clock edge that data must be stable

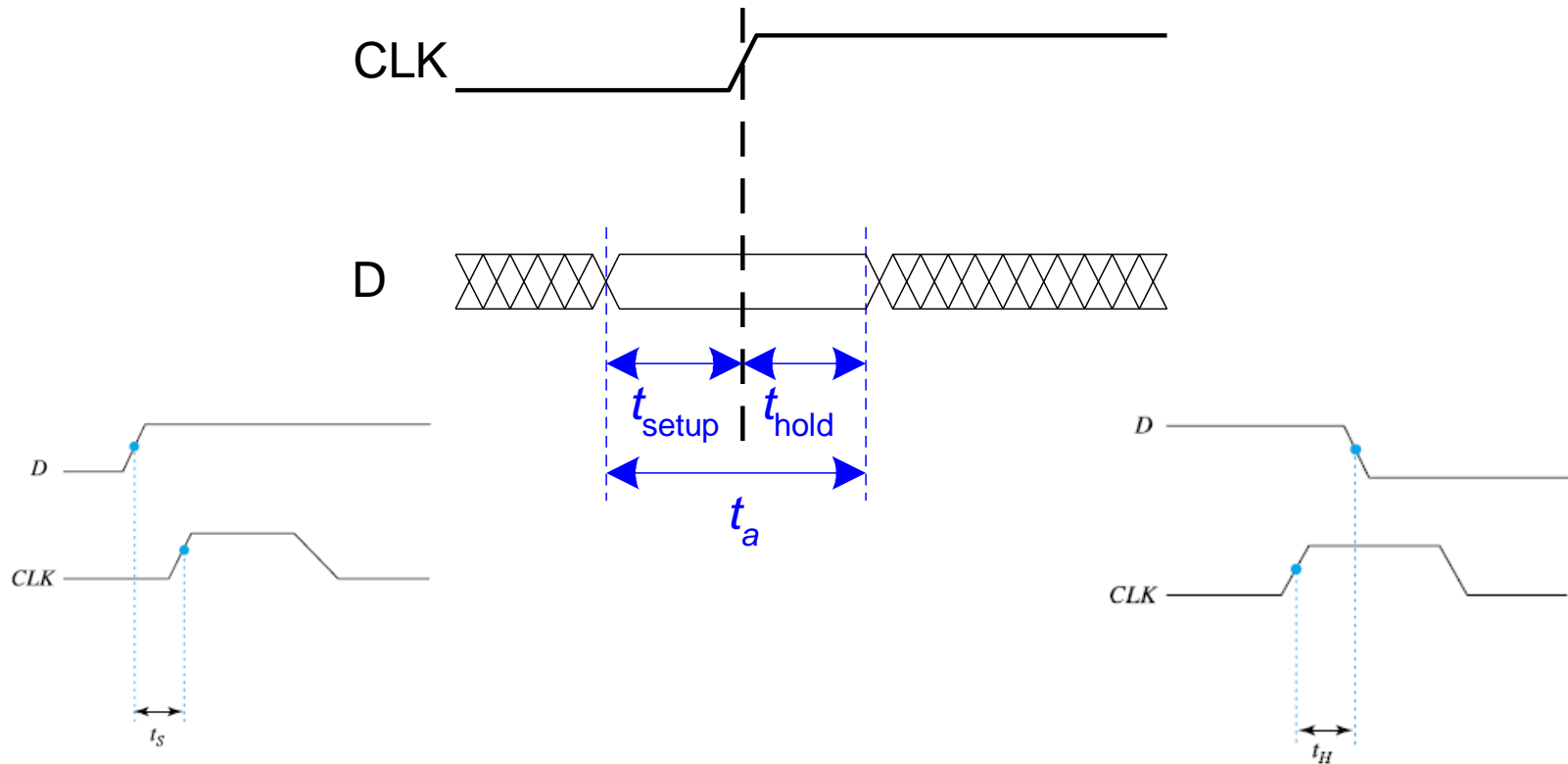
# Input Timing Constraints

- Hold time: Aperture time(간극 시간):
- $t_a$  = time around clock edge that data must be stable
- ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )


 
# Output Timing

- Propagation delay:  $t_{pcq}$  = time after clock edge that the output  $Q$  is guaranteed to be stable (i.e., to stop changing)
- Contamination delay:  $t_{ccq}$  = time after clock edge that  $Q$  might be unstable (i.e., start changing)




# Dynamic Discipline

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.  
(클럭 에지의 Contamination  $t_{ccq}$  동안 안정화되어야 한다)
- Specifically, the input must be stable
  - at least  $t_{\text{setup}}$  before the clock edge
  - at least until  $t_{\text{hold}}$  after the clock edge
 
# Dynamic Discipline


- The delay between registers has a minimum and maximum delay, dependent on the delays of the circuit elements




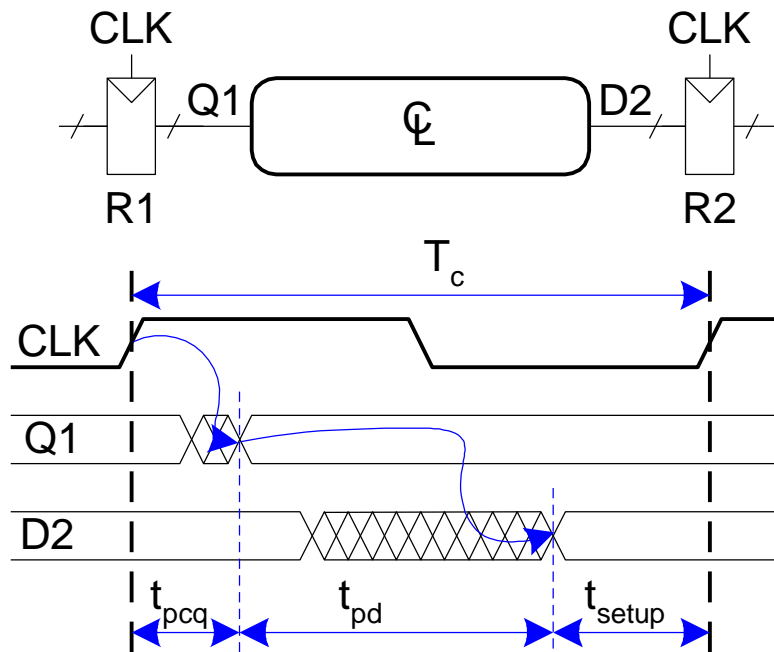
# Setup Time Constraint (준비시간제한)


- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic. ( $t_{pd}$  = 최대지연제한(준비시간제한))
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.



$$T_{c(\text{최소클럭주기})} \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd(\text{최대지연제한})} \leq T_c - (t_{pcq} + t_{\text{setup}})$$
 
# Hold Time Constraint (대기시간제한)


- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{ccq} + t_{cd} > t_{\text{hold}}$$

$$T_{cd(\text{최소혼합지연})} > t_{\text{hold}} - t_{ccq}$$

# Timing Analysis

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$


$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

# Timing Analysis

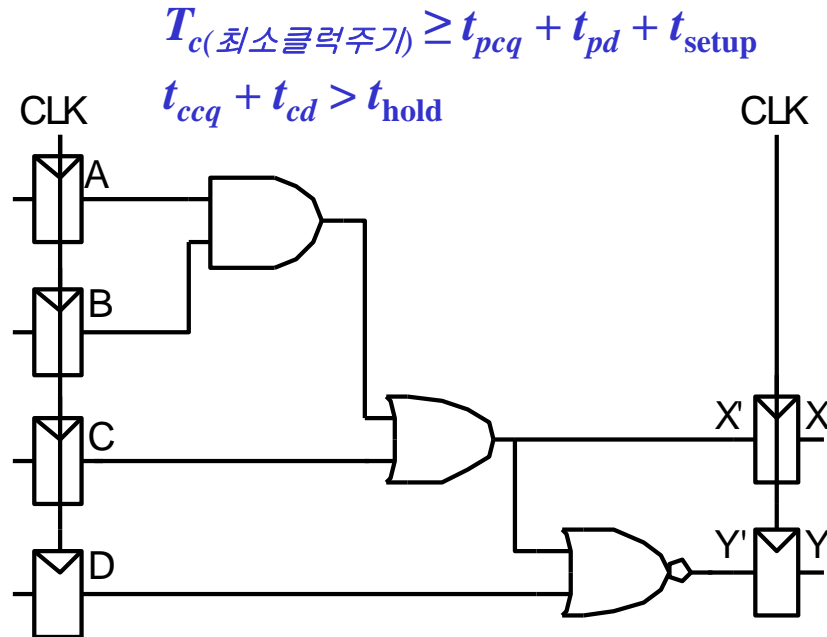

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 175 \text{ ps}$$

$$f_c = 1/T_c = 5.7 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$


Hold time constraint:

$$t_{ccq} + t_{pd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$

# Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 175 \text{ ps}$$

$$f_c = 1/T_c = 5.7 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$


Hold time constraint:

$$t_{ccq} + t_{pd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$

 
### 3.5.3 Clock Skew(클록 시차)

- The clock doesn't arrive at all registers at the same time  
(클록이 모든 레지스터에 같은 시간에 도달하지 않는다)
- This may be caused by delay or other timing noise (딜레이나 노이즈 때문에)
- **Skew** is the difference between two clock edges
- Because there may be many registers in a system, we examine the worst case for each case to guarantee that the dynamic discipline is not violated for any register


 
# Setup Time Constraint with Clock Skew


- In the worst case, the CLK2 is earlier than CLK1



$$T_c - t_{skew} \geq t_{pcq} + t_{pd} + t_{setup}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$
 
# Hold Time Constraint with Clock Skew

- In the worst case, CLK2 is later than CLK1





$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$

$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$



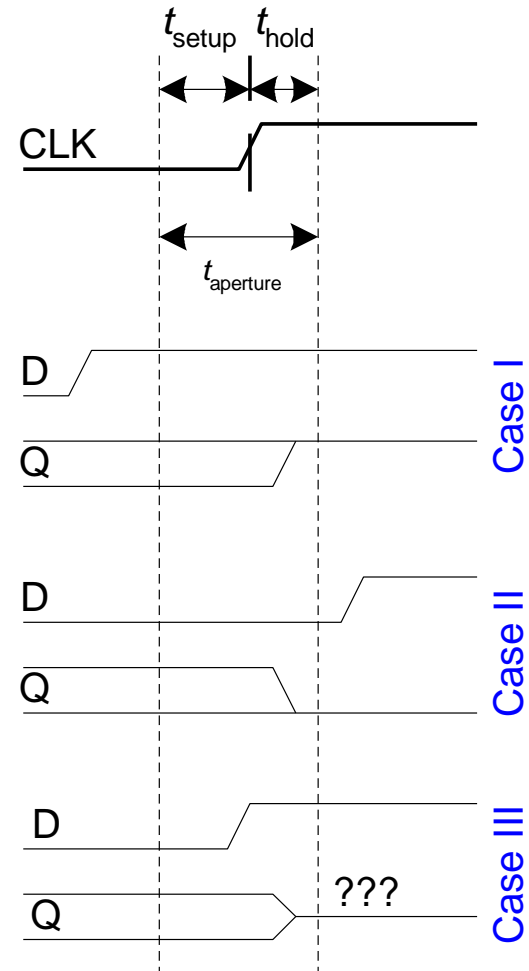 
# Violating the Dynamic Discipline

- Asynchronous (for example, user) inputs might violate the dynamic discipline



 
# Metastability(준안정 상태)

- Any **bistable device** has two stable states and a metastable state between them (안정상태와 준안정상태)
- A **flip-flop** has two stable states (1 and 0) and one metastable state
- If a flip-flop gets stuck in the metastable state, it could stay there for an undetermined amount of time


 
# Flip-flop Internals

- Because the flip-flop has feedback, if  $Q$  is somewhere between 1 and 0, the cross-coupled nand gates will eventually drive the output to either rail (1 or 0, depending on which one it is closer to).



- A signal is considered metastable if it hasn't resolved to 1 or 0
- The probability that the output  $Q$  is still metastable after waiting a time,  $t$ , is:

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

$t_{\text{res}}$  : time to resolve to 1 or 0

$T_0, \tau$  : properties of the circuit

# Metastability

- Intuitively:
  - $T_0/T_c$  describes the probability that the input changes at a bad time, i.e., during the aperture time

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$


- $\tau$  is a time constant indicating how fast the flip-flop moves away from the metastable state; it is related to the delay through the cross-coupled gates in the flip-flop

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- In short, if a flip-flop samples a metastable input, if you wait long enough ( $t$ ), the output will have resolved to 1 or 0 with high probability.

 
### 3.5.5 Synchronizers(동기화기)

- **Asynchronous inputs ( $D$ ) are inevitable** (user interfaces, systems with different clocks interacting, etc.).  
(비동기 입력은 필연적이다)
- The **goal of a synchronizer** is to make the probability of failure (the output  $Q$  still being metastable) low.
- A synchronizer cannot make the probability of failure 0.


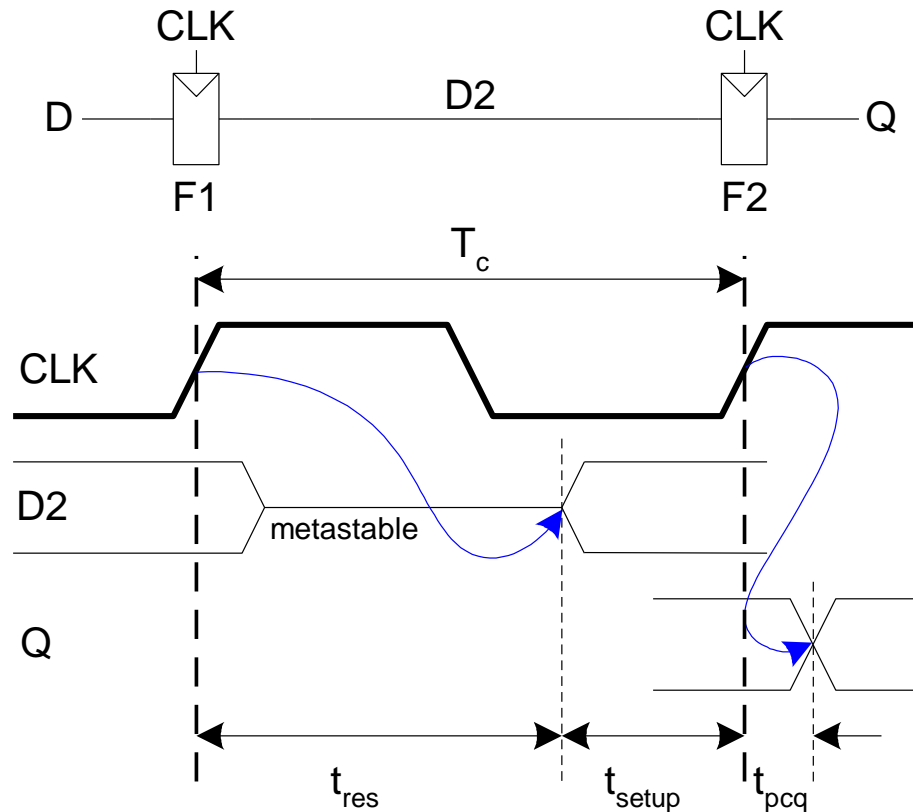
## 3.5.5 Synchronizer Internals(동기화기 내부)


- A **synchronizer** can be built with two back-to-back flip-flops.
- Suppose the input D is transitioning when it is sampled by flip-flop 1, F1.
- The amount of time the internal signal D2 can resolve to a 1 or 0 is  $(T_c - t_{\text{setup}})$ .


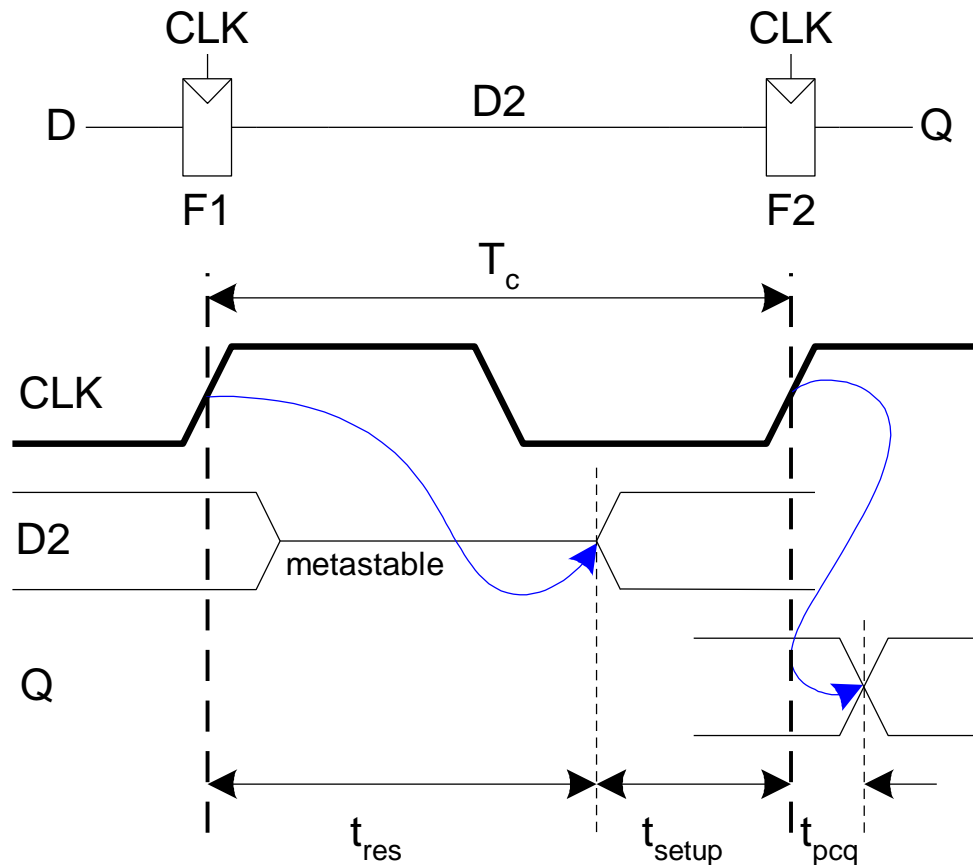
# Synchronizer Probability of Failure

For each sample, the probability of failure of this synchronizer is:

$$P(\text{failure}) = (T_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$



# Synchronizer Mean Time Before Failure

- If the asynchronous input changes once per second, the probability of failure per second of the synchronizer is simply  $P(\text{failure})$ :
- In general, if the input changes  $N$  times per second, the probability of failure per second of the synchronizer is:


$$P(\text{failure})/\text{second} = (NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

- Thus, the synchronizer fails, on average,  $1/[P(\text{failure})/\text{second}]$
- This is called the *mean time between failures*, MTBF:

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] = (T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$



# Example Synchronizer

 

- Suppose:  
 $T_c = 1/500 \text{ MHz} \tau = 200 \text{ ps}$   
 $T_0 = 150 \text{ ps}$   
 $N = 1 \text{ time per second}$   
 $t_{\text{setup}} = 100 \text{ ps}$
- What is the probability of failure? MTBF?  
$$P(\text{failure}) = (150 \text{ ps} / 2 \text{ ns}) e^{-(1.9 \text{ ns}) / 200 \text{ ps}}$$
$$= 5.6 \times 10^{-6}$$
$$P(\text{failure}) / \text{second} = 1 (5.6 \times 10^{-6})$$
$$= 5.6 \times 10^{-6} / \text{second}$$
$$\text{MTBF} = 1 / [P(\text{failure}) / \text{second}] \approx 50 \text{ hours}$$

## 3.6 Parallelism (병렬 처리)

- Some definitions:
  - Token: **A group** of inputs processed to produce a group of outputs  
(출력그룹을 생성하기 위해 처리되는 입력그룹)
  - Latency(잠복시간): Time for one token to pass **from start to end**
  - Throughput(처리량): **The number of tokens** that can be produced per unit time
- The purpose of parallelism is to increase throughput.
- Two types of parallelism:
  - **Spatial parallelism** (공간 병렬 처리)
    - duplicate hardware performs multiple tasks at once
  - **Temporal parallelism** (시간 병렬 처리)
    - task is broken into multiple stages
    - also called pipelining
    - for example, an assembly line

# Parallelism Example

- Ben Bitdiddle is baking cookies to celebrate the installation of his traffic light controller.
- It takes 5 minutes to roll the cookies and 15 minutes to bake them.
- After finishing one batch he immediately starts the next batch.
- What is the latency and throughput if Ben doesn't use parallelism?


Latency = 5 + 15 = 20 minutes = 1/3 hour

Throughput = 1 tray/ 1/3 hour = 3 trays/hour

# Parallelism Example

- What is the latency and throughput if Ben uses parallelism?
  - **Spatial parallelism:** Ben asks Allysa P. Hacker to help, using her own oven
  - **Temporal parallelism:** Ben breaks the task into two stages: roll and baking. He uses two trays. While the first batch is baking he rolls the second batch, and so on.


# Spatial Parallelism

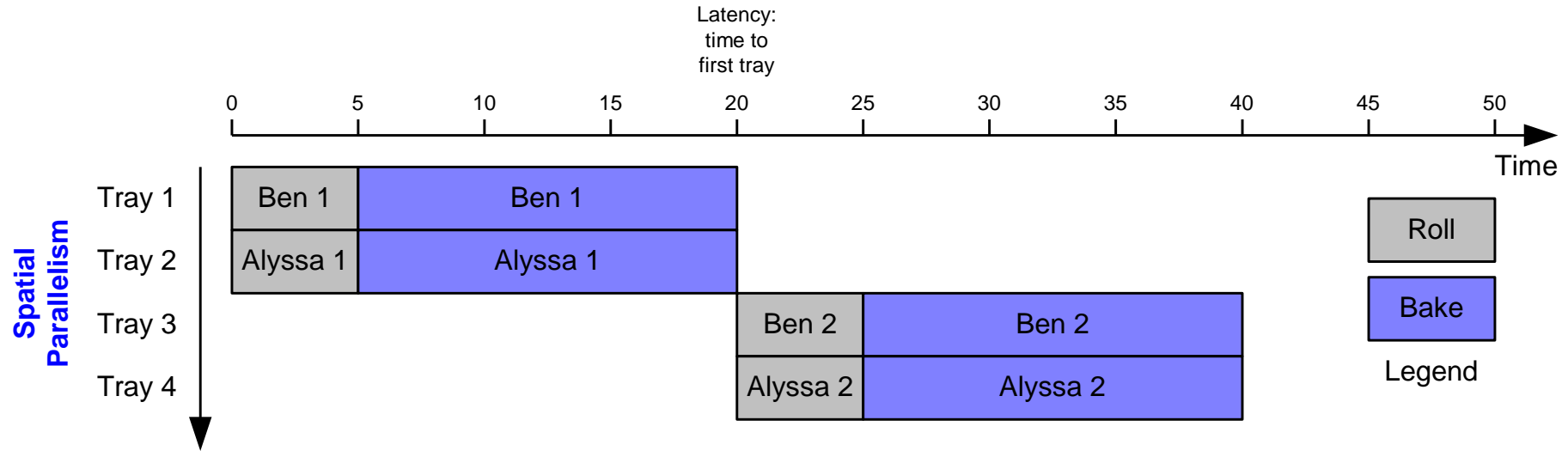

Latency = 5 + 15 = 20 minutes =  $\frac{1}{3}$  hour

Throughput = 2 trays /  $\frac{1}{3}$  hour = 6 trays/hour

# Temporal Parallelism


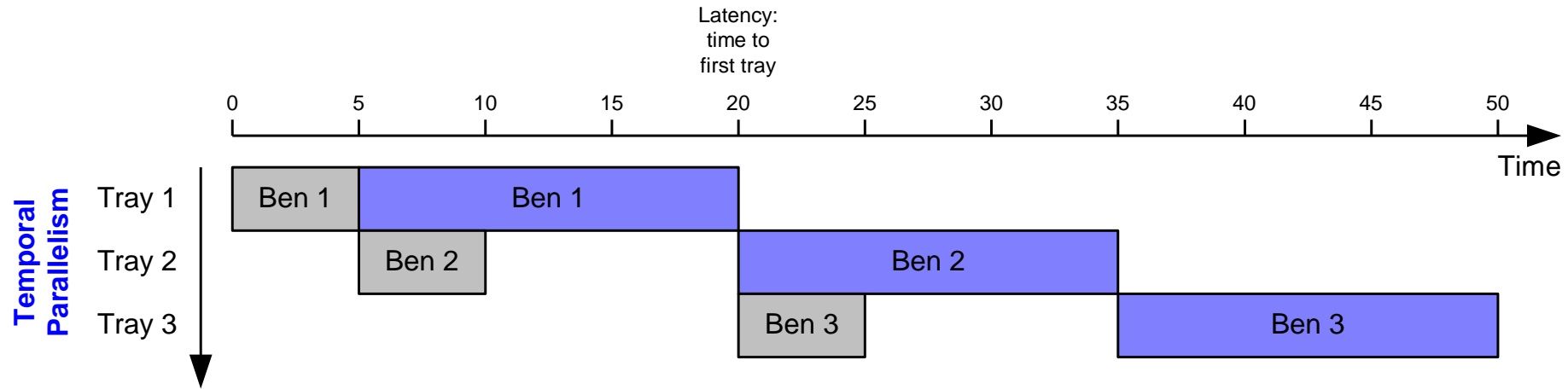


Latency =  $5 + 15 = 20$  minutes =  $\frac{1}{3}$  hour

Throughput =  $1 \text{ trays} / \frac{1}{4} \text{ hour} = 4 \text{ trays/hour}$

Using both techniques, the throughput would be  $8 \text{ trays/hour}$

# 파이프라인 프로세서

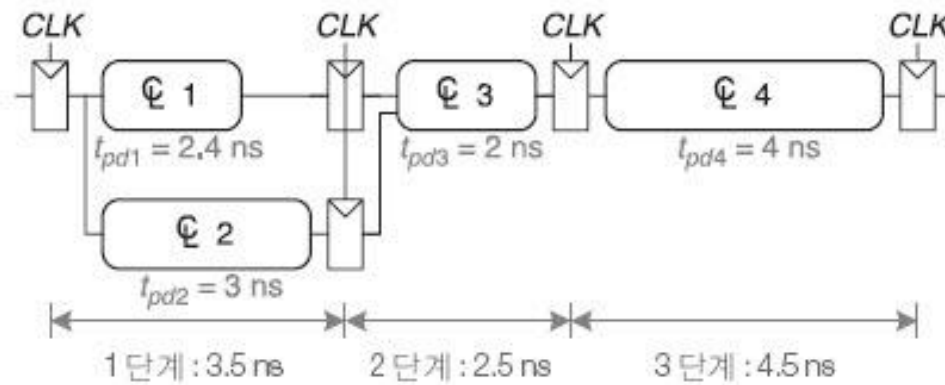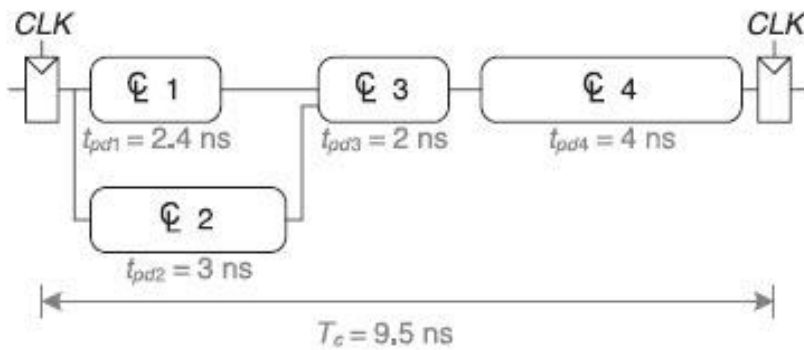

# Q & A

