


Chapter 2 :: Combinational Logic Design

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 2 :: Topics

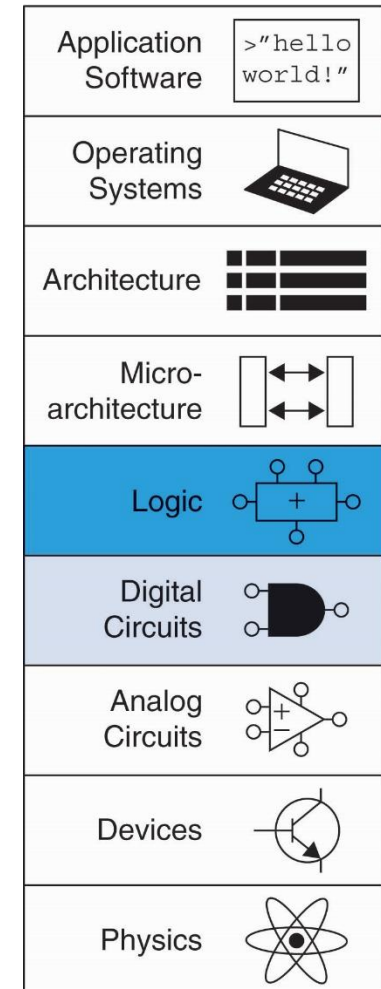
- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing



Introduction


A logic circuit is composed of:

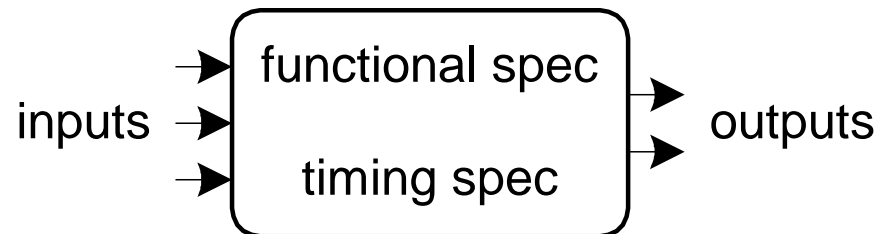- Inputs
- Outputs
- Functional specification
- Timing specification




Circuits

 - Nodes
 - Inputs: A, B, C
 - Outputs: Y, Z
 - Internal: $n1$
- Circuit elements
 - $E1, E2, E3$
 - Each a circuit




Types of Logic Circuits

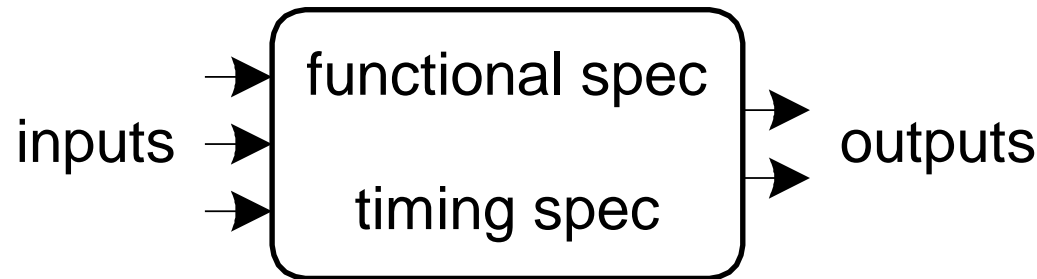- Combinational Logic
 - Memoryless
 - Outputs determined by current values of inputs
- Sequential Logic
 - Has memory
 - Outputs determined by previous and current values of inputs



Rules of Combinational Composition

 - Every circuit element is itself **combinational**
- Every node of the circuit is either designated as an input to the circuit or connects to **exactly one output** terminal of a circuit element
- The circuit contains **no cyclic paths**: every path through the circuit visits each circuit node at most once
- **Example:**




2.2 Boolean Equations (부울식)

- Functional specification of outputs in terms of inputs
- Example:

$$S = F(A, B, C_{\text{in}})$$
 
$$C_{\text{out}} = F(A, B, C_{\text{in}})$$



$$S = A \oplus B \oplus C_{\text{in}}$$
$$C_{\text{out}} = AB + AC_{\text{in}} + BC_{\text{in}}$$

Equations (기본 논리식의 표현)

- 기본적인 불 대수식은 AND, OR, NOT을 이용하여 표현
- AND 식은 곱셈의 형식으로 표현하고, OR 식은 덧셈의 형식으로 표현
- NOT 식은 \overline{X} 또는 X' 로 표현
- 완전한 논리식은 입력 항목들의 상태에 따른 출력을 결정하는 식

- $X=0$ and $Y=1$ 일 때 출력을 1로 만들려는 경우 출력 논리식

$$F = \overline{X}Y$$

- $X=0$ or $Y=1$ 일 때 출력을 1로 만들려는 경우 출력 논리식

$$F = \overline{X} + Y$$

- $(X=0 \text{ and } Y=1) \text{ or } (X=1 \text{ and } Y=0)$ 일 때 출력을 1로 만들려는 경우
출력 논리식

$$F = \overline{X}Y + X\overline{Y}$$

Sum-of-Products (SOP) Form (곱의 합 형태)

- All Boolean equations can be written in SOP form
- Each row in a truth table has a **minterm**(함수에 모든 변수를 포함)
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- The function is formed by ORing the minterms for which the output is TRUE
- Thus, a sum (OR) of products (AND terms)
 - (1 단계는 AND항(곱의 항, product term)으로 구성되고,)
 - (2 단계는 OR항(합의 항, sum term)으로 만들어진 논리식)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B, C) = \overline{A}B + AB = \Sigma(1, 3)$$

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row in a truth table has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- The function is formed by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)
(1단계는 OR항(합의 항, sum term)으로 구성되고,
(2 단계는 AND항(곱의 항, product term)으로 만들어진 논리식)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B, C) = (A + B)(\overline{A} + \overline{B}) = \Pi(0, 2)$$

Some Definitions

- Minterm: product that includes all input variables
 $ABC', AB'C, A'BC'$
- Maxterm: sum that includes all input variables
 $(A'+B'+C), (A'+B+C'), (A+B'+C)$

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch (\overline{E})
 - If it's not open (\overline{O}) or
 - If they only serve corndogs (C)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = OC'$$

$$= \Sigma(2)$$

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O+C)(O+C')(O'+C')$$

$$= \Pi(0, 1, 3)$$

2.3 Boolean Algebra (부울 대수)

- Set of axioms and theorems to **simplify** Boolean equations
(부울식을 간단히 하기 위해 부울 대수를 사용한다.)
- Like regular algebra, but in some cases simpler because variables can have **only two values** (1 or 0)
- Axioms and theorems obey the principles of **duality**:
 - ANDs and ORs interchanged, 0's and 1's interchanged



Boolean Axioms and Theorems

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements



T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

  



T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

  


T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

  



T4: Identity Theorem

- $\overline{\overline{B}} = B$

 

T5: Complement Theorem

  - $B \cdot \overline{B} = 0$
- $B + \overline{B} = 1$



Boolean Theorems of Several Variables

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2})$	De Morgan's Theorem

Simplifying Boolean Expressions: Example 1

- $Y = A\bar{B} + AB$

$$= A(B + \bar{B}) \quad \text{T8}$$

$$= A(1) \quad \text{T5'}$$

$$= A \quad \text{T1}$$

Simplifying Boolean Expressions: Example 2

- $Y = A(AB + ABC)$

$$= A(AB(1 + C)) \quad \text{T8}$$

$$= A(AB(1)) \quad \text{T2'}$$

$$= A(AB) \quad \text{T1}$$

$$= (AA)B \quad \text{T7}$$

$$= AB \quad \text{T3}$$


Examples

- 진리표로부터 SOP(sum-of-products(최소항식)) 형태로 논리식을 표현하고 식을 간소화 하시오. 또한 게이트 회로를 설계 하시오.

입력		출력
a	b	f
0	0	0
0	1	1
1	0	1
1	1	1



$$\Rightarrow f = \bar{a}b + a\bar{b} + ab$$
 
$$\begin{aligned} f &= a'b + ab' + ab + ab \\ &= a(b' + b) + b(a' + a) \\ &= a + b \end{aligned}$$





DeMorgan's Theorem

  - $Y = \overline{AB} = \overline{A} + \overline{B}$



  
- $Y = \overline{\overline{A} + \overline{B}} = \overline{A} \cdot \overline{B}$



Bubble Pushing

 2.5.2 Bubble Pushing (버블 추가)

- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.




- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.




Bubble Pushing

 - What is the Boolean expression for this circuit?



Bubble Pushing

 
- What is the Boolean expression for this circuit?






$$Y = AB + CD$$

Bubble Pushing Rules

 
- Begin at the output of the circuit and work toward the inputs.
(출력부분에서 시작하여 입력 부분으로 진행)
- Push any bubbles on the final output back toward the inputs.
- Working backward, draw each gate in a form so that bubbles cancel.



Bubble Pushing Rules

   

 
$$Y = \overline{A} \overline{B} C + \overline{D}$$



 2.4 From Logic to Gates (논리에서 게이트로)

- Two-level logic: ANDs followed by Ors
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$
- Schematic(개요도)
 - 서로 연결된 선과 요소를 보여주는 digital 회로의 diagram




Circuit Schematic Rules (개요도 작성 규칙)

- Inputs are on the left (or top) side of a schematic
(입력은 개요도의 왼쪽이나 위쪽에 있다.)
- Outputs are on the right (or bottom) side of a schematic
(출력은 개요도의 오른쪽이나 아래쪽에 있다.)
- Whenever possible, gates should flow from left to right
(개요도는 왼쪽에서 오른쪽으로 흐른다.)
- Straight wires are better to use than wires with multiple corners
(가능한 꺾이선보다는 곧은 직선을 사용한다.)


Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
(선은 항상 T 접합으로 연결한다.)
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction

 

wires connect
at a dot


 


 wires crossing
without a dot do
not connect



Priority Circuit Hardware (예제 2.7)

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 
 


진리표에서의 X는
Don't care(무관항)

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

  2.5 Multiple Output Circuits(다단계 조합논리)

- 하드웨어 축소
 - 다단계 조합논리는 더 적은 하드웨어를 사용할 수 있다.
 - $A \oplus B \oplus C = (A \oplus B) \oplus C$



2.6 Don't Cares


- 진리표에서의 X는 Don't care(무관항)

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Contention: X

 
- 회로에서의 X는 Contention(경쟁)
 - circuit tries to drive the output to 1 and 0
 - 금지값 or 잘 알려지지 않은 값



Floating: Z

- Floating(부동값) Z : high나 low로 구동되지 않음.
- Said to be Floating, high impedance, open, high Z
- Output is not connected to the input

Tristate Buffer

 

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

2.7 Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
- (부울식을 간단히 하기 위하여 그래프로 나타내는 방법)
- $PA + P\bar{A} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

K-map Example

Y C \ AB		00	01	11	10
		0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

K-Map

Y C \ AB		00	01	11	10
		0	0	1	0
	1	0	1	0	1


$$Y = AB + \bar{A}\bar{B}C$$

K-map Rules

- Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction. (각각의 원은 2의 제곱형태의 크기를 가진 직사각형 블록으로)
- Each circle must be as large as possible (각각의 원은 가능한 크게)
- A circle may wrap around the edges of the K-map (원은 맵의 가장자리를 둘러쌀 수 있고)
- A one in a K-map may be circled multiple times (1은 여러 원에 묶일 수도 있고)
- A “don't care” (X) is circled only if it helps minimize the equation (X는 식을 최소화한다면 묶고)

Karnaugh Maps 간략화 예

<i>a</i>	<i>b</i>	<i>f</i>
0	0	1
0	1	1
1	0	1
1	1	0

 

Karnaugh Maps 간략화 예

$\backslash BC$	00	01	11	10
A 0	1	1		
A 1			1	1

$$F = \overline{A}\overline{B} + AB$$

$\backslash BC$	00	01	11	10
A 0	1			1
A 1				

$$F = \overline{A}\overline{C}$$

양쪽 끝은
연결되어 있다.

$\backslash BC$	00	01	11	10
A 0		1	1	
A 1		1	1	

$$F = C$$

$\backslash BC$	00	01	11	10
A 0	1	1	1	1
A 1				




$$F = \overline{A}$$

$\backslash BC$	00	01	11	10
A 0	1			1
A 1	1			1

$$F = \overline{C}$$


양쪽 끝은
연결되어 있다.

Karnaugh Maps 간략화 예

   


세 번 중복하여 묶었다.


Karnaugh Maps 간략화 예

 


$$F = BD + \overline{B}\overline{D}$$

 

$$F = \overline{B} + \overline{D}$$

 

$$F = \overline{A} + \overline{B}$$

 

$$F = \overline{A}\overline{B} + \overline{A}\overline{D} + \overline{A}C + \overline{B}C$$

K-Maps with Don't Cares


Y CD \ AB		AB			
		00	01	11	10
00	00	1	0	X	1
	01	0	X	X	1
	11	1	1	X	X
	10	1	1	X	X

$$Y = A + \bar{B}\bar{D} + C$$

K-Maps 예제



- 다음 진리표로부터 카르노 맵을 작성하고 간략화하여라.

$A B C D$	F
0 0 0 0	x
0 0 0 1	1
0 0 1 0	x
0 0 1 1	1
0 1 0 0	x
0 1 0 1	1
0 1 1 0	1
0 1 1 1	1
1 0 0 0	0
1 0 0 1	0
1 0 1 0	0
1 0 1 1	0
1 1 0 0	0
1 1 0 1	1
1 1 1 0	1
1 1 1 1	0

 

$$F(A, B, C, D) = \bar{A} + \bar{B}CD + B\bar{C}\bar{D}$$

예제 2.10) 7-세그먼트 디코더

  

© 2007 Elsevier, Inc. All rights reserved



Table 2.6 Seven-segment display decoder truth table

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	0	0	1	1
others	0	0	0	0	0	0	0

예제 2.10

Table 2.6 Seven-segment display decoder truth table

$D_{3:0}$	S_a	S_b	S_c	S_d	S_e	S_f	S_g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1					
0100	0	1					
0101	1	0					
0110	1	0					
0111	1	1					
1000	1	1					
1001	1	1					
others	0	0					

  

2.8 Combinational Building Blocks

- full-adder (전가산기) : 그림 2.5 참조
- Multiplexers
- Decoders


Half-Adder

- Half-Adder (반가산기)란?
 - 두 개의 2진수 한자리를 입력(X, Y)하여 합(Sum)과 자리올림수(Carry)를 얻는 덧셈 논리회로
 - 반가산기는 더하기 수행 시 자리올림을 무시
 - 예를 들어 $5+6$ 의 내용을 입력하면 반가산기의 출력은 올림자리는 무시하고 10이 출력됨
 - 자리올림을 포함하는 계산을 위해서는 전가산기를 사용해야 함

Half-Adder 논리식과 진리표

$$\begin{array}{r}
 X \\
 + Y \\
 \hline
 C \quad S
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0 \quad 0
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 0 \quad 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 0 \quad 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 1 \quad 0
 \end{array}$$

입력		출력	
X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


 


$$S = \overline{X}Y + X\overline{Y} = X \oplus Y$$

$$C = X \cdot Y$$

Half-Adder 논리회로

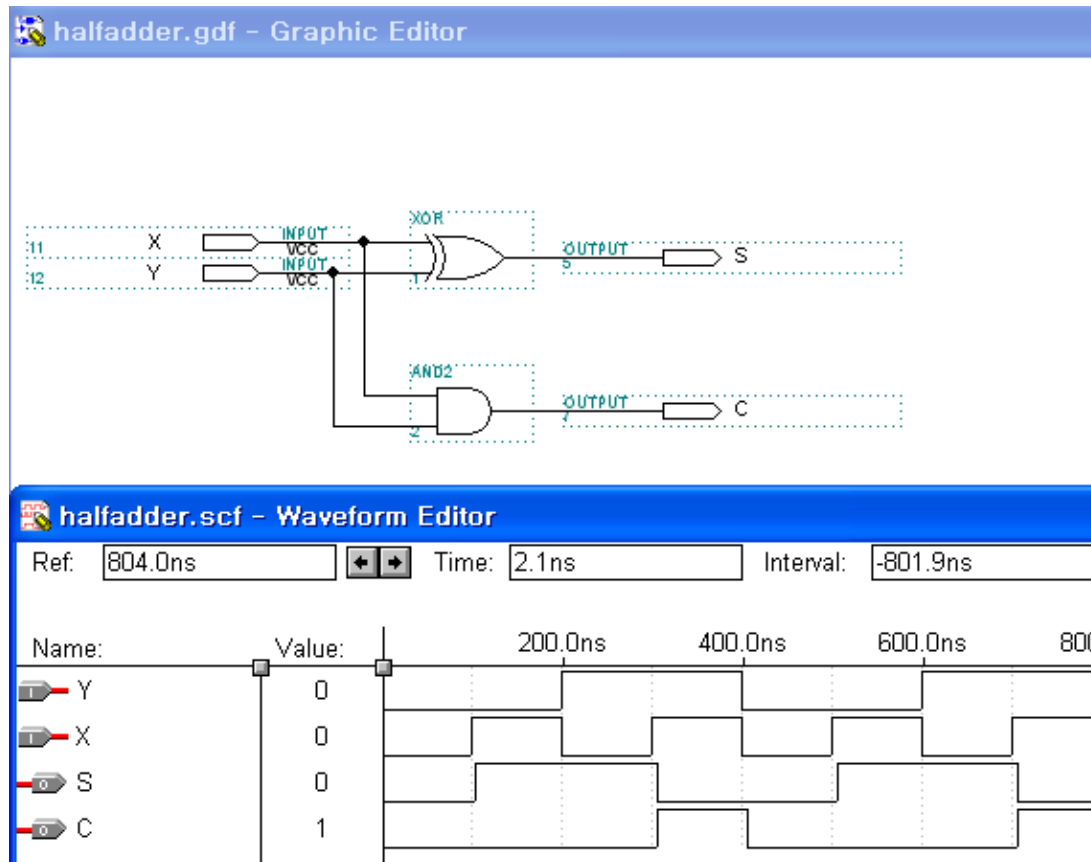 - 논리회로 작성 및 컴파일
- Timing Simulation 결과 파형



Full-Adder

- Full-Adder(전가산기)란?
 - 두 개의 2진수 입력(X , Y)과 하위 자리에서 발생한 자리올림수(Carry_{in})를 포함하여 한 자리수 2진수 세 개의 입력 비트들의 덧셈을 수행하여 합(Sum)과 자리올림수($\text{Carry}_{\text{out}}$)를 얻는 논리회로

Full-Adder 논리식과 진리표



입력			출력	
X	Y	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(a) 진리표

$$S = X \oplus Y \oplus C_{in}$$


$$C_{out} = XY + (X \oplus Y)C_{in}$$

(b) 논리식

 
 


(c) 논리기호

Full-Adder 논리회로

 

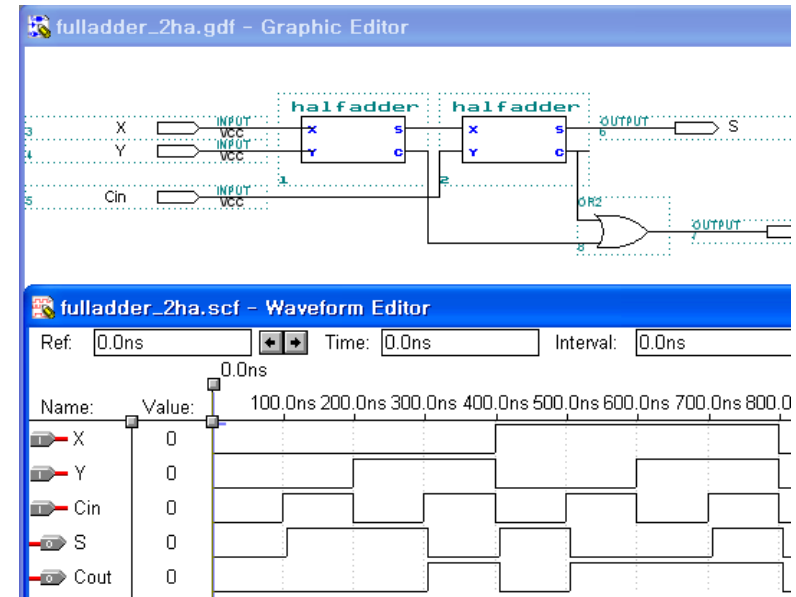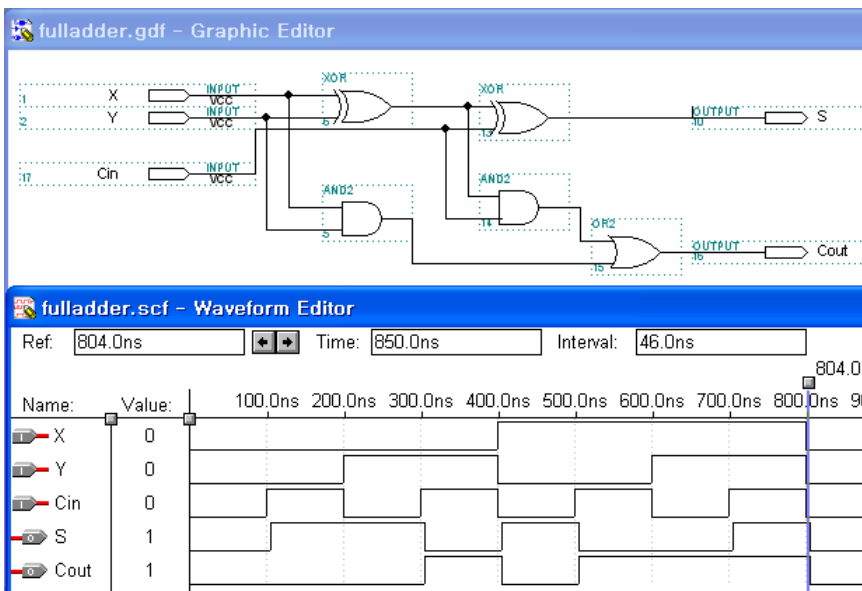
- 논리회로 작성 및 컴파일
- Timing Simulation 결과 파형
 - 조합논리회로사용, HalfAdder 두 개 사용)



 2.8.1 Multiplexer (Mux)

- Selects between one of N inputs to connect to the output.
(여러 가지 가능한 입력 중에서 출력을 선택)

- $\log_2 N$ -bit select input – control input



- Example: 2:1 Mux

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


2:1 Mux

- **Logic gates**

- Sum-of-products form



Y S	D _{1:0}			
	00	01	11	10
0	0	1	1	0
1	0	0	1	1

$$Y = D_0 \bar{S} + D_1 S$$


 


- **Tristates**

  
- For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




4:1 Mux

  

(a)

 

(b)

 


(c)

Logic using Multiplexers



- Using the mux as a lookup table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

 


- Reducing the size of the mux

  

예제 2.12, 13

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$
 (a)



A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


(a)

(b)

 


 2.8.2 Decoders

- N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 


Logic using Decoders

- OR minterms
- XNOR

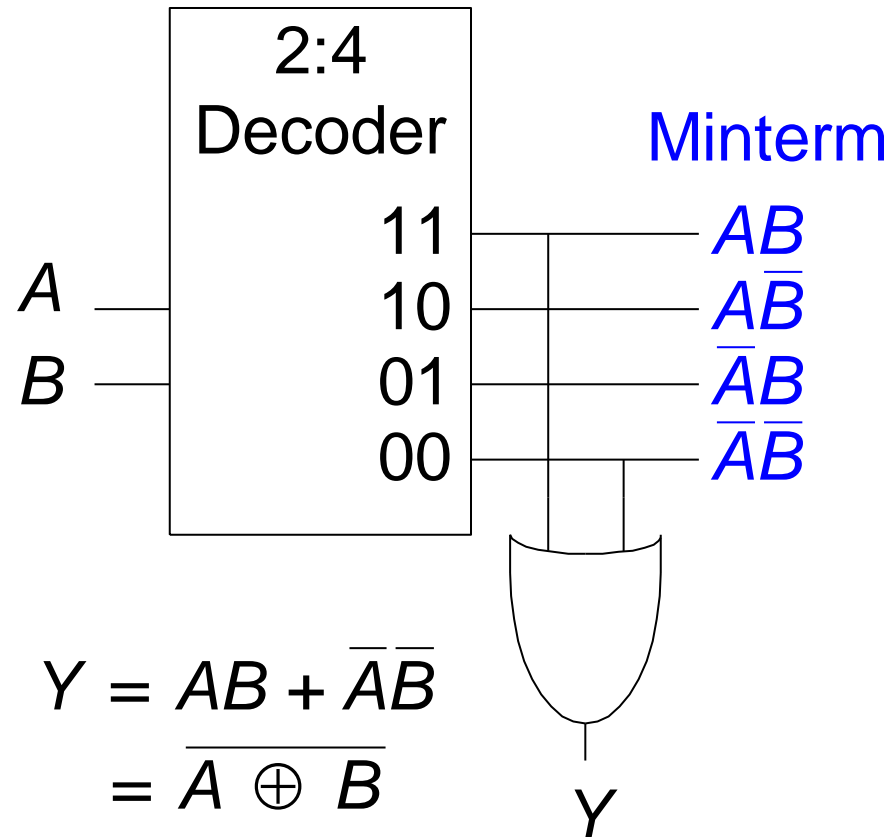

 
2.9 Timing

- Delay between input change and output changing
- One of the biggest challenges in circuit design: making the circuit fast



Propagation & Contamination Delay

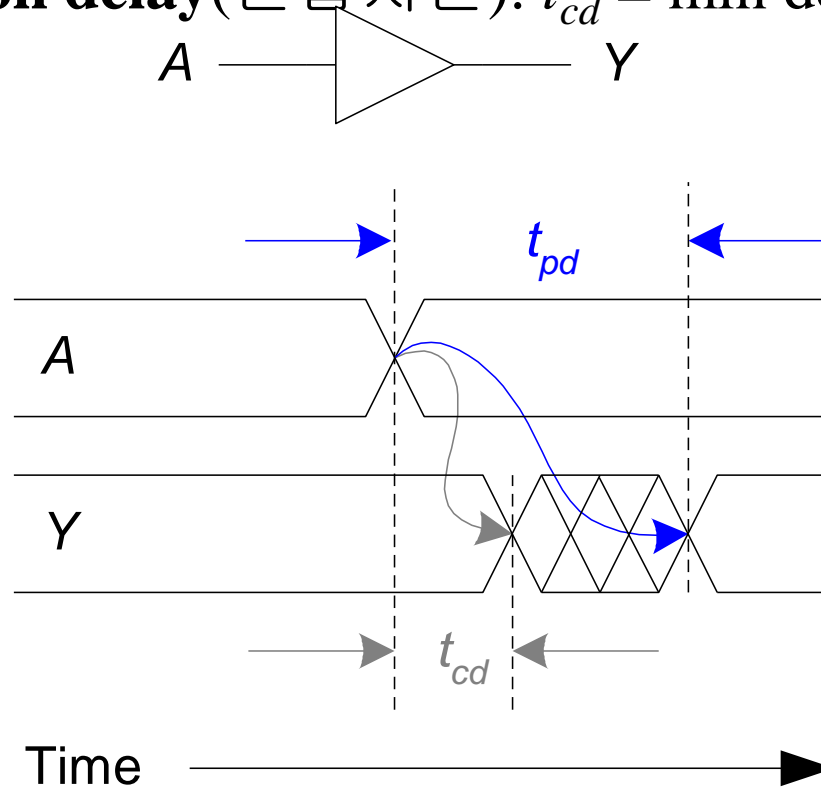
- **Propagation delay**(전파 지연): $t_{pd} = \max$ delay from input to output
- **Contamination delay**(혼합 지연): $t_{cd} = \min$ delay from input to output



Propagation & Contamination Delay

- Delay is caused by
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- Reasons why t_{pd} and t_{cd} may be different:
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold

Critical and Short Paths

 


Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$

Short Path: $t_{cd} = t_{cd_AND}$

Glitch, Why Understand Glitches?

- A **glitch** occurs when a single input change causes multiple output changes
(글리치는 하나의 입력변화가 다수의 출력변화의 원인이 될 때 발생)
- Glitches don't cause problems because of **synchronous design** conventions (which we'll talk about in Chapter 3)
- But it's important to **recognize a glitch** when you see one in simulations or on an oscilloscope
(글리치의 존재를 인식하는 것이 중요하다)
- **Can't get rid of all glitches** – simultaneous transitions on multiple inputs can also cause glitches



Glitch Example

 

		<i>AB</i>			
		00	01	11	10
<i>C</i>	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

 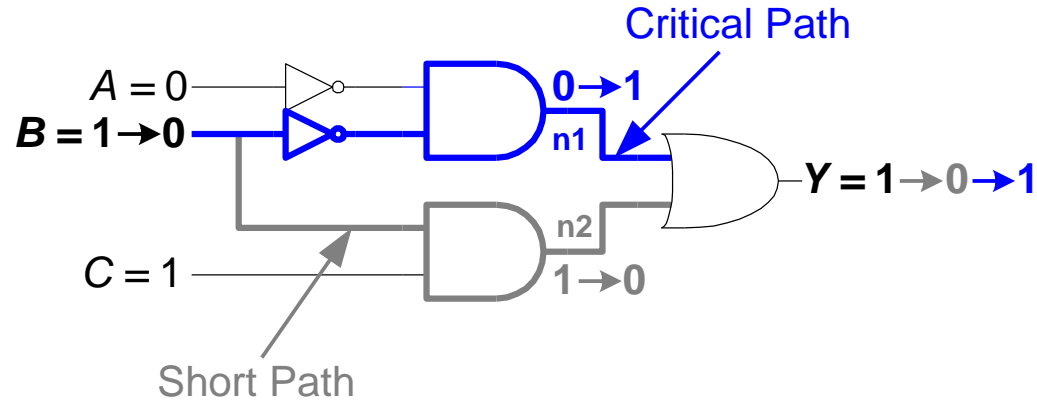


Glitch Example (cont.)

Y C	AB			
	00	01	11	10
0	1	0	0	0
1	1	1	1	0

$\bar{A}\bar{C}$

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

 

Q & A

